

2. Answer the following :

2×4=8

- (a) What are peak value and mean value of alternating current?
- (b) What do you mean by thermocouple and thermo-e.m.f.?
- (c) What are magnetic flux and magnetic flux density?
- (d) Write the relation between true power and power factor.

3. Answer any *three* from the following : 5×3=15

- (a) Calculate the value of the torque on a current loop placed in a uniform magnetic field.
- (b) An e.m.f. of 10 volts is applied to a circuit having a resistance of 10 ohms and an inductance of 0.5 henry. Find the time required by the current to attain 63.2 % of its final value. What is the time constant of the circuit?
- (c) A capacitor of capacitance 0.1  $\mu\text{F}$  is first charged and then discharged through a resistance of 10 megaohms. Find the time, the potential will take to fall to half its original value.

(d) The e.m.f. of a thermocouple, one junction of which is kept at  $0^{\circ}\text{C}$ , is given by  $E = bt + ct^2$ . Find the neutral temperature and the Peltier and Thomson coefficient.

(e) (i) What do you mean by mutual and self-inductance? 2

(ii) Two coils, a primary of 600 turns and a secondary of 30 turns are wound on an iron ring of radius 0.1 m and cross-section  $4 \times 10^{-2}$  m diameter. Find their mutual inductance ( $\mu$  for iron = 800). 3

4. Answer any *three* from the following :  $10 \times 3 = 30$

(a) Define the current density at any point. Derive an expression for current density. Prove the equation of continuity

$$\text{div } J + \frac{dy}{dt} = 0$$

(b) An alternating e.m.f. is applied to a circuit containing an inductor, capacitor and resistor in series. Obtain expression for the current, impedance and phase of current. Obtain the condition for the current to be a resonance with the applied e.m.f. Obtain the resonance frequency.

- (d) The e.m.f. of a thermocouple, one junction of which is kept at  $0^{\circ}\text{C}$ , is given by  $E = bt + ct^2$ . Find the neutral temperature and the Peltier and Thomson coefficient.
- (e) (i) What do you mean by mutual and self-inductance? 2
- (ii) Two coils, a primary of 600 turns and a secondary of 30 turns are wound on an iron ring of radius 0.1 m and cross-section  $4 \times 10^{-2}$  m diameter. Find their mutual inductance ( $\mu$  for iron = 800). 3

4. Answer any *three* from the following :  $10 \times 3 = 30$

- (a) Define the current density at any point. Derive an expression for current density. Prove the equation of continuity

$$\text{div } J + \frac{dy}{dt} = 0$$

- (b) An alternating e.m.f. is applied to a circuit containing an inductor, capacitor and resistor in series. Obtain expression for the current, impedance and phase of current. Obtain the condition for the current to be a resonance with the applied e.m.f. Obtain the resonance frequency.

- (c) A charge capacitor of capacitance  $C$  discharges through a circuit containing of a coil of inductance  $L$  and a resistance  $R$ . Find the charge on the capacitor in  $t$  sec after it starts discharging. Deduce the condition under which the discharge is oscillatory. Find the period and frequency of the oscillatory discharge, where  $R$  is very small.
- (d) State Biot-Savart law. Using Biot-Savart law, calculate the value of magnetic field due to an infinitely long straight wire carrying a current  $i$  amp at a distance  $d$  from the wire.
- (e) Write a short note on any *one* of the following :
- (i) Transformer
  - (ii) Anderson's bridge

\*\*\*